


Lab 7

Useful Components

Connor Aksama – 1778028


State diagrams derived from the 3-bit and 4-bit LFSRs.

3-bit LFSR State Diagram

 

The state diagram for the 3-bit LFSR, which uses the XNOR of the 2 most significant bits to produce the next least significant bit. Each state transition labeled with a "*" is followed on each clock edge. The starting state for this state machine is "000".

4-bit LFSR State Diagram

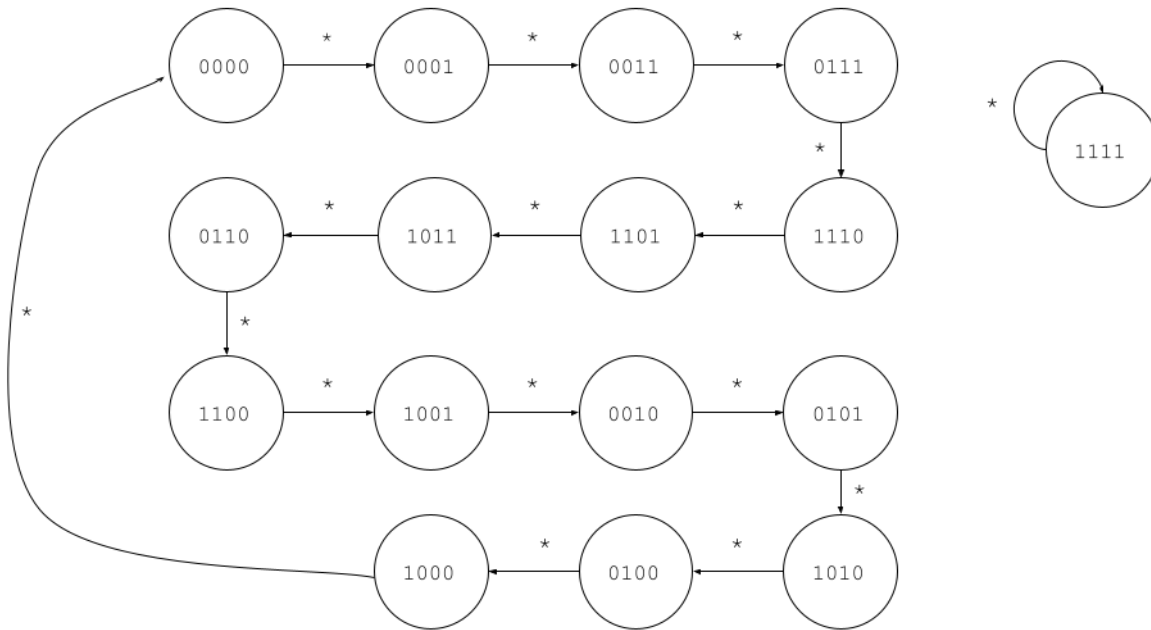

The state diagram for the 4-bit LFSR, which uses the XNOR of the 2 most significant bits to produce the next least significant bit. Each state transition labeled with a “*” is followed on each clock edge. The starting state for this state machine is “0000”.

Simulation of your working 10-bit adder that covers the 6 situations described.


10-bit Adder Simulation

+	sum	12	420	511	0	14	-500	12
+	a	-512	420	64	0	-1	511	-512
+	b	-500	0	447	0	15	13	-500

The simulation for the 10-bit adder, demonstrating (in order): (1) an addition where one input is 0, (2) an addition whose result is 511, (3) an addition whose result is 0, (4) an example of unsigned overflow (-1 [signed] is equivalent to 1023 [unsigned]), (5) an example of positive signed overflow, and (6) an example of negative signed overflow.

Simulation of your working 3-bit counter.


3-bit Counter Simulation

 

The simulation for the 3-bit counter showing that every clock cycle where a “win” input is received, the count increases by 1, and that the count stays the same when a “win” input is not received.

Simulation of your working 9-bit LFSR with the state cycle length indicated.

9-bit LFSR Simulation

 

The simulation for the 9-bit LFSR. The “out” signal shows the output of the LFSR, and the “i” counter shows the number of states visited by the LFSR. The initial state of the LFSR is 9'b0, and the simulation is set to stop once it loops back to the initial state. Notice that in the bottom screenshot, the simulation reaches 511 unique states before coming back to the initial 9'b0 state and stopping.

A screenshot of the “Resource Utilization by Entity” page, showing your design’s computed size.

Analysis & Synthesis Resource Utilization by Entity										
<<Filter>>										
	Compilation Hierarchy Node	Combinational ALUTs	Dedicated Logic Registers	Block Memory Bits	DSP Blocks	Pins	Virtual Pins	Full Hierarchy Name	Entity Name	Library Name
1	▼ tug_of_war	60 (1)	48 (0)	0	0	39	0	tug_of_war	tug_of_war	work
1	▼ adder10:adder	8 (0)	0 (0)	0	0	0	0	tug_of_war_adder10:adder	adder10	work
1	full_adder:d3	3 (3)	0 (0)	0	0	0	0	tug_of_war_adder10:adder_full_adder:d3	full_adder	work
2	full_adder:d4	1 (1)	0 (0)	0	0	0	0	tug_of_war_adder10:adder_full_adder:d4	full_adder	work
3	full_adder:d7	3 (3)	0 (0)	0	0	0	0	tug_of_war_adder10:adder_full_adder:d7	full_adder	work
4	full_adder:d8	1 (1)	0 (0)	0	0	0	0	tug_of_war_adder10:adder_full_adder:d8	full_adder	work
2	center_light:c0	1 (1)	1 (1)	0	0	0	0	tug_of_war_center_light:c0	center_light	work
3	clock_divider:div	16 (16)	16 (16)	0	0	0	0	tug_of_war_clock_divider:div	clock_divider	work
4	dff_3:d0	1 (1)	2 (2)	0	0	0	0	tug_of_war_dff_3:d0	dff_3	work
5	dff_3:d1	0 (0)	2 (2)	0	0	0	0	tug_of_war_dff_3:d1	dff_3	work
6	lfsr_9:l9	1 (1)	9 (9)	0	0	0	0	tug_of_war_lfsr_9:l9	lfsr_9	work
7	normal_light:l1	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:l1	normal_light	work
8	normal_light:l2	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:l2	normal_light	work
9	normal_light:l3	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:l3	normal_light	work
10	normal_light:l4	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:l4	normal_light	work
11	normal_light:r1	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:r1	normal_light	work
12	normal_light:r2	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:r2	normal_light	work
13	normal_light:r3	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:r3	normal_light	work
14	normal_light:r4	1 (1)	1 (1)	0	0	0	0	tug_of_war_normal_light:r4	normal_light	work
15	▼ player_scores:scores	20 (0)	6 (0)	0	0	0	0	tug_of_war_player_scores:scores	player_scores	work
1	counter:p1	3 (3)	3 (3)	0	0	0	0	tug_of_war_player_scores_counter:p1	counter	work
2	counter:p2	3 (3)	3 (3)	0	0	0	0	tug_of_war_player_scores_counter:p2	counter	work
3	▼ double_seg7:scores	14 (0)	0 (0)	0	0	0	0	tug_of_war_double_seg7:scores	double_seg7	work
1	seg7:d0	7 (7)	0 (0)	0	0	0	0	tug_of_war_double_seg7_seg7:d0	seg7	work
2	seg7:d1	7 (7)	0 (0)	0	0	0	0	tug_of_war_double_seg7_seg7:d1	seg7	work
16	user_input:right_press	2 (2)	2 (2)	0	0	0	0	tug_of_war_user_input:right_press	user_input	work
17	victory:v0	2 (2)	2 (2)	0	0	0	0	tug_of_war_victory:v0	victory	work

Resource utilization for the tug_of_war top-level module.

Time Estimation

This lab took approximately 7 hours, in total, to complete.